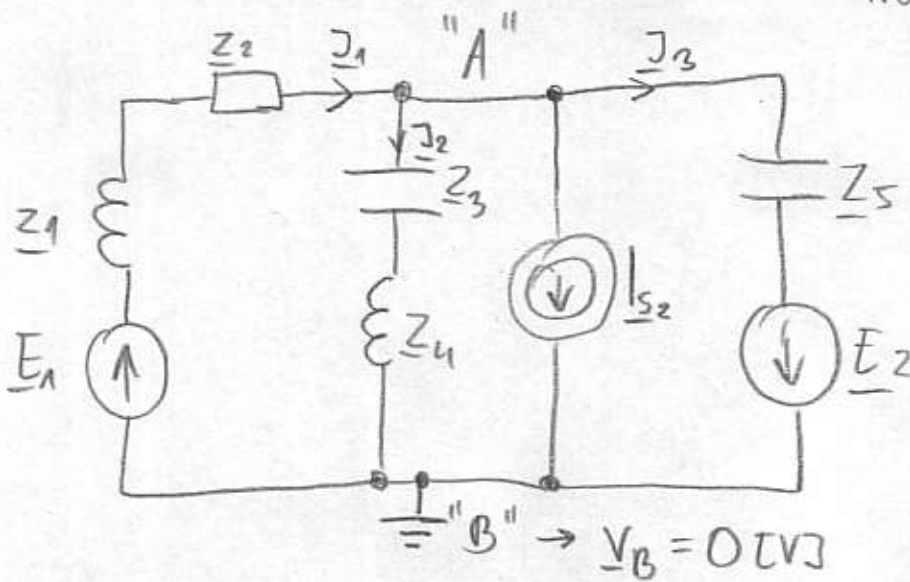



NODE VOLTAGE METHOD



$$Z_u = 1[\Omega]$$

$$u = \{1, 2, 3, 4, 5\}$$

CIRCUIT AFTER TRANSFORMATION

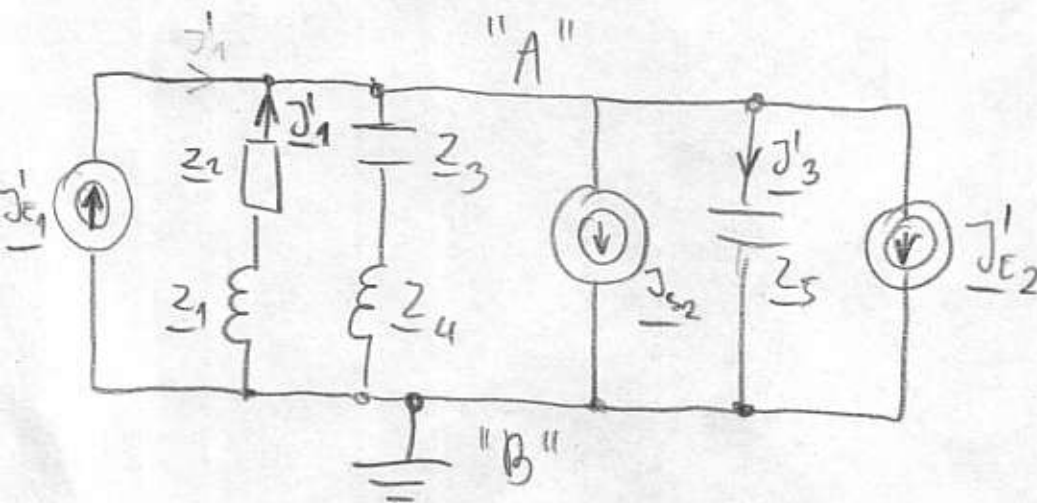

$$J'_{E1} = E_1 \cdot Y_{12}$$

$$Y_{12} = \frac{1}{Z_{12}} = \frac{1}{Z_1 + Z_2}$$

$$J'_{E2} = E_2 \cdot Y_5$$

$$Y_{34} = \frac{1}{Z_{34}} = \frac{1}{Z_3 + Z_4}$$

$$\sum (I_s)_{A''} = J'_{E1} - J_{s2} - J'_{E2} = V_A (Y_{12} + Y_{34} + Y_5) - \underbrace{V_B \cdot (Y_{12} + Y_{34} + Y_5)}_{0'' \rightarrow V_B = 0}$$

$$J'_{E1} - J_{s2} - J'_{E2} = V_A \cdot (Y_{12} + Y_{34} + Y_5)$$

$$E_1 \cdot Y_{12} - J_{s2} - E_2 \cdot Y_5 = V_A \cdot (Y_{12} + Y_{34} + Y_5)$$

$$V_A = \frac{E_1 \cdot Y_{12} - J_{s2} - E_2 \cdot Y_5}{Y_{12} + Y_{34} + Y_5}$$

$$J_1 = J'_1 + J'_{E1} = (V_A - V_B) \cdot Y_{12} + E_1 \cdot Y_{12} = V_A \cdot Y_{12} + E_1 \cdot Y_{12}$$

$$J_2 = (V_A - V_B) \cdot Y_{34} = V_A \cdot Y_{34}$$

$$J_3 = J'_3 + J'_{E2} = (V_A - V_B) \cdot Y_5 + E_2 \cdot Y_5 = V_A \cdot Y_5 + E_2 \cdot Y_5$$