

Zastosowanie praw Kirchhoffa w obwodzie prądu zmiennego

Wyznaczanie prądów w gałęziach obwodu prądu przemiennego sinusoidalnie zmiennego.

$$\underline{V}_s = 10 + j \cdot 5 [V] = \sqrt{10^2 + 5^2} \cdot e^{j \cdot \arctan \frac{5}{10}} [V] = \sqrt{125} \cdot e^{-j \frac{\pi}{4}} [A]$$

$$\underline{I} = 1 [A]$$


$$|Z_{L1}| = 5 [\Omega] \rightarrow Z_{L1} = j \cdot 5 [\Omega]$$

$$|Z_{L2}| = 2 [\Omega] \rightarrow Z_{L2} = j \cdot 2 [\Omega]$$

$$|Z_{C1}| = 1 [\Omega] \rightarrow Z_{C1} = -j [\Omega]$$

$$|Z_{R1}| = 1 [\Omega] \rightarrow Z_{R1} = 1 [\Omega]$$

$$|Z_{R2}| = 1 [\Omega] \rightarrow Z_{R2} = 1 [\Omega]$$

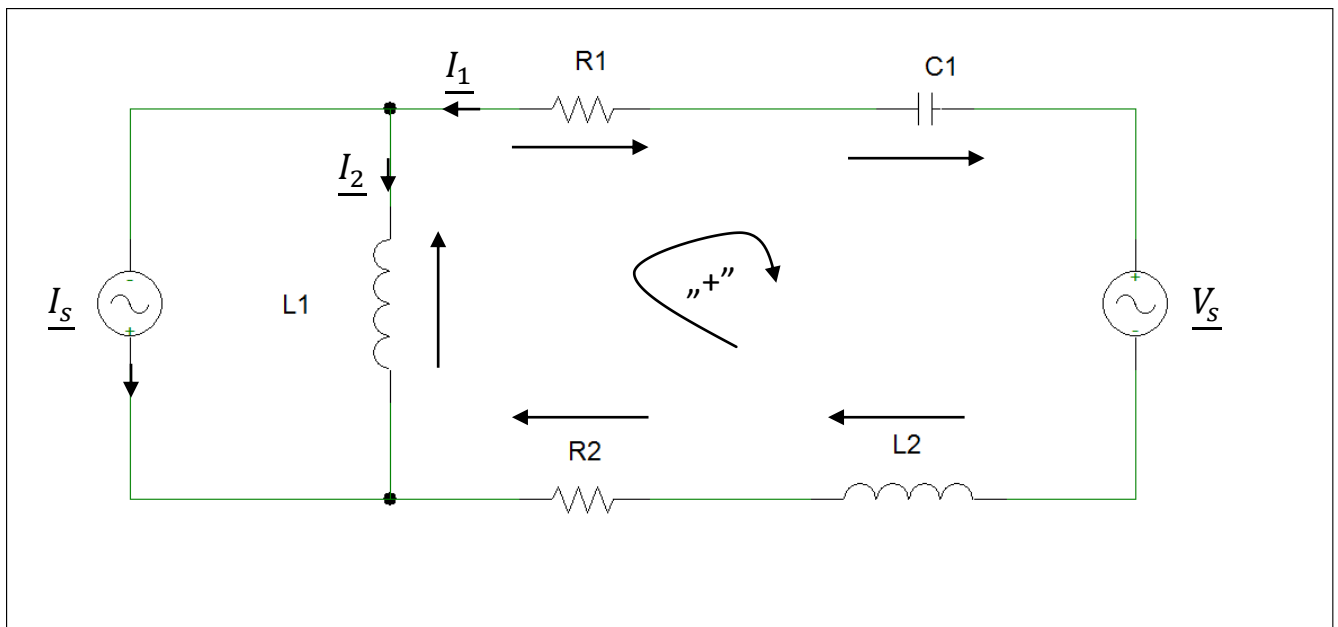

Rysunek 1. Obwód prądu zmiennego.

Pierwsze prawo Kirchhoffa

$$\underline{I}_1 - \underline{I}_2 - \underline{I}_s = 0$$

Drugie prawo Kirchhoffa

$$\underline{I}_2 \cdot \underline{Z}_{L1} + \underline{I}_1 \cdot \underline{Z}_{R1} + \underline{I}_1 \cdot \underline{Z}_{C1} - \underline{V}_s + \underline{I}_1 \cdot \underline{Z}_{R2} + \underline{I}_1 \cdot \underline{Z}_{L2} = 0$$

$$\underline{I}_2 = \underline{I}_1 - \underline{I}_s$$

$$\underline{I}_2 \cdot \underline{Z}_{L1} + \underline{I}_1 \cdot (\underline{Z}_{R1} + \underline{Z}_{C1} + \underline{Z}_{R2} + \underline{Z}_{L2}) - \underline{V}_s = 0$$

$$(\underline{I}_1 - \underline{I}_s) \cdot \underline{Z}_{L1} + \underline{I}_1 \cdot (\underline{Z}_{R1} + \underline{Z}_{C1} + \underline{Z}_{R2} + \underline{Z}_{L2}) - \underline{V}_s = 0$$

$$-\underline{I}_s \cdot \underline{Z}_{L1} + \underline{I}_1 \cdot (\underline{Z}_{R1} + \underline{Z}_{C1} + \underline{Z}_{R2} + \underline{Z}_{L2} + \underline{Z}_{L1}) - \underline{V}_s = 0$$

$$\underline{I}_1 = \frac{\underline{V}_s + \underline{I}_s \cdot \underline{Z}_{L1}}{\underline{Z}_{R1} + \underline{Z}_{C1} + \underline{Z}_{R2} + \underline{Z}_{L2} + \underline{Z}_{L1}}$$

$$\underline{I}_1 = \frac{\underline{V}_s + \underline{I}_s \cdot \underline{Z}_{L1}}{\underline{Z}_{R1} + \underline{Z}_{C1} + \underline{Z}_{R2} + \underline{Z}_{L2} + \underline{Z}_{L1}}$$

$$\underline{I}_1 = \frac{10 + j \cdot 5 + 1}{1 - j + 1 + j \cdot 2 + j \cdot 5} = \frac{11 + j \cdot 5}{2 + j \cdot 6}$$

$$\underline{I}_1 = \frac{11 + j \cdot 5}{2 + j \cdot 6} \cdot \frac{2 - j \cdot 6}{2 - j \cdot 6} = \frac{22 - j \cdot 66 + j \cdot 10 - (-1) \cdot 30}{4 - j \cdot 12 + j \cdot 12 + 36}$$

$$\underline{I}_1 = \frac{52 - j \cdot 56}{40} [A]$$

$$I_1 = \sqrt{\left(\frac{52}{40}\right)^2 + \left(\frac{56}{40}\right)^2} = 1,91[A]$$

$$\underline{I}_2 = \underline{I}_1 - \underline{I}_s$$

$$\underline{I}_2 = \frac{52 - j \cdot 56}{40} - 1 = \frac{12 - j \cdot 56}{40} [A]$$

$$I_1 = \sqrt{\left(\frac{12}{40}\right)^2 + \left(\frac{56}{40}\right)^2} = 1,43[A]$$