


15.18

Dane:

$R_w = 0,5 \Omega$

$E = 1,5 V$

$R = 1000 \Omega$

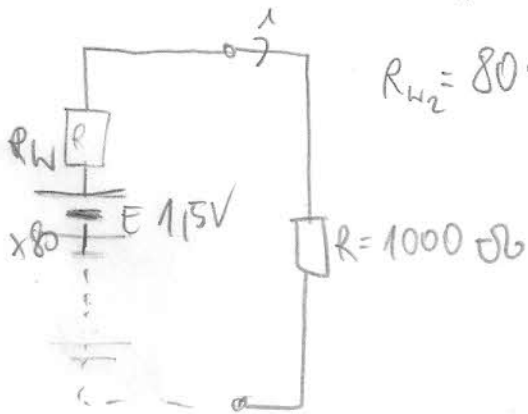

$R_{w2} = 80 \cdot 0,5 \Omega$

$E_2 = 80 \cdot 1,5 V$

$$i = \frac{E_2}{R_{w2} + R} = \frac{80 \cdot 1,5}{80 \cdot 0,5 + 1000} = \frac{120}{1040} \approx 0,12 A$$

$$i \approx 0,12 A \quad \checkmark$$

15.19

Dane: $i = 2,5 A$; $U = 220 V$

$t = 6 h$

$P = ?$

$E = ?$

$P = U \cdot i = 2,5 \cdot 220 = 550 W$

$P = 550 W \quad \checkmark$

$P = 0,55 kW \quad \checkmark$

$E = 0,55 \cdot 6 = 3,3 kWh \quad \checkmark$

$E = 3,3 kWh \quad \checkmark$

15.20

1) $P_1 = 40 W$

2) $P_2 = 100 W$

$U = 220 V$

$P = U \cdot i$

$i_1 = \frac{P_1}{U} = \frac{40}{220} \approx 0,18 A$

$i_2 = \frac{P_2}{U} = \frac{100}{220} \approx 0,45 A$

$U = R \cdot i$

$i_2 = 0,45 A \quad \checkmark$

$P = i^2 \cdot R$

$i_1 = 0,18 A \quad \checkmark$

$R_1 = \frac{P_1}{i_1^2} = \frac{40}{(0,18)^2} = 1234,6 \Omega$


$R_2 = \frac{P_2}{i_2^2} = \frac{100}{(0,45)^2} \approx 494 \Omega$

$R_1 = 1234,6 \Omega \quad \checkmark$

$R_2 = 494 \Omega \quad \checkmark$

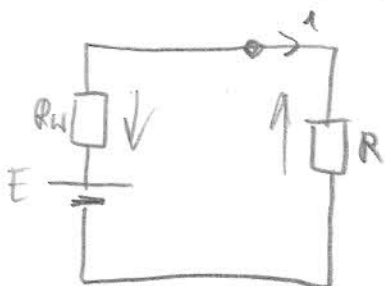15.21

Dane: $E = 1,08 V$ $R_w = 2 \Omega$ $R_0 = 8 \Omega$ $t = 1 s$



$$i = \frac{E}{R_w + R_0} = \frac{1,08}{2 + 8} = \frac{1,08}{10} = 0,108 [A]$$

$E = i^2 \cdot R_0 \cdot t = 0,108^2 \cdot 8 \cdot 1 = 0,864 J$

$E = 0,864 J \quad \checkmark$

$R = R_w + R_0$