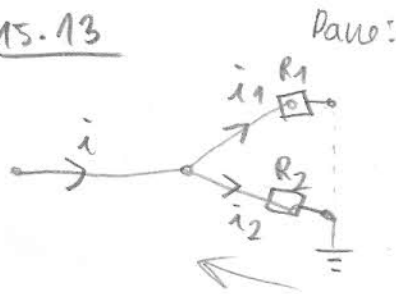


15.13



Dane:

$$i = 1,2 \text{ A}$$

$$U = i_1 \cdot R_1$$

$$R_1 = 4,8 \text{ } \Omega$$

$$i = i_1 + i_2$$

$$U = i_2 \cdot R_2$$

$$R_2 = 7,2 \text{ } \Omega$$

$$i = U \cdot G$$

$$G = \frac{1}{4,8} + \frac{1}{7,2} \text{ [S]}$$

$$i_1 = \frac{U}{R_1} \quad i_2 = \frac{U}{R_2}$$

$$i = \frac{U}{R_1} + \frac{U}{R_2}$$

$$U = i_1 \cdot R_1 \quad U = i_2 \cdot R_2$$

$$U = i \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$i = \frac{U \cdot R_2}{R_1 \cdot R_2} + \frac{U \cdot R_1}{R_1 \cdot R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{R_2}{R_1 \cdot R_2} + \frac{R_1}{R_1 \cdot R_2}$$

$$\frac{1}{R} = \frac{R_1 + R_2}{R_1 \cdot R_2}$$

$$R = \frac{R_1 \cdot R_2}{R_1 + R_2} \text{ [} \frac{\Omega \cdot \Omega}{\Omega} \text{]}$$

$$i \cdot \frac{R_1 \cdot R_2}{R_1 + R_2} = i_1 \cdot R_1 \quad | : R_1$$


$$i_1 = \frac{R_2}{R_1 + R_2} \cdot i$$

$$i_1 = 0,6 i$$

$$i_2 = 0,4 i$$

$$i_1 = 0,72 \text{ A} \quad i_2 = 0,48 \text{ A} \quad \checkmark$$

15.14

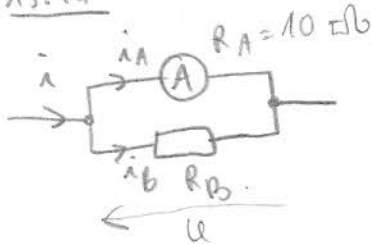

$$i_{A \text{ max}} = 3 \text{ mA} = 3 \cdot 10^{-3} \text{ A}$$

$$i = 1,5 \text{ A}$$

$$i = U \cdot \frac{R_A + R_B}{R_A \cdot R_B}$$

$$i_A = \frac{U}{R_A}$$

$$i_B = \frac{U}{R_B}$$

$$U = i \cdot \frac{R_A \cdot R_B}{R_A + R_B}$$

$$U = i_A \cdot R_A$$

$$i_A \cdot R_A = i \cdot \frac{R_A \cdot R_B}{R_A + R_B} \quad | : R_A$$

$$i_A = i \cdot \frac{R_B}{R_A + R_B}$$

$$i_A (R_A + R_B) = i \cdot R_B \quad | : R_B$$

$$i_A \cdot \frac{(R_A + R_B)}{R_B} = i \quad | : i_A$$

$$\frac{R_A}{R_B} + \frac{R_B}{R_B} = \frac{i}{i_A}$$

$$\frac{R_A}{R_B} + 1 = \frac{i}{i_A}$$

$$\frac{R_A}{R_B} = \frac{i}{i_A} - 1 \quad | : R_A$$


$$\frac{1}{R_B} = \frac{(\frac{i}{i_A} - 1)}{R_A}$$

$$R_B = \frac{R_A}{(\frac{i}{i_A} - 1)}$$

$$R_B \approx 0,2 \text{ } \Omega$$

← rezystancja boczniaka

15.15

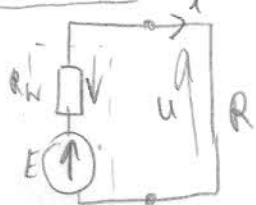

$$i = \frac{E}{R_W + R}$$

$$i = \frac{1,08}{1,5 + 12} = 0,08 \text{ A}$$

$$i = 0,08 \text{ A} \quad \checkmark$$

$$E = 1,08 \text{ V} \quad R_W = 1,5 \Omega \quad R = 12 \Omega$$


$$U = E - i \cdot R_W$$

$$U = 1,08 - 0,08 \cdot 1,5$$

$$U = 1,08 - 0,12$$

$$U = 0,96 \text{ V} \quad \checkmark$$

15.16

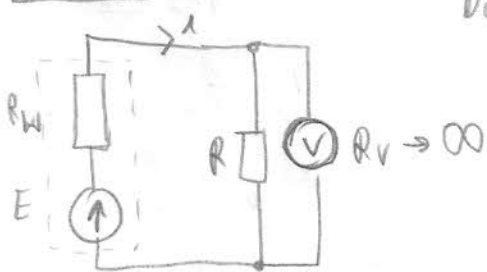

Dane: $i = 0,2 \text{ A}$ $R_W = 0,6 \Omega$ $U = 1,8 \text{ V}$

$$i = \frac{E}{R_W + R}$$

$$U = E - i \cdot R_W \quad U = i \cdot R$$

$$\downarrow$$


$$E = U + i \cdot R_W$$

$$E = 1,8 + 0,2 \cdot 0,6$$

$$E = 1,8 + 0,12 = 1,92 \text{ V}$$

$$E = 1,92 \text{ V} \quad \checkmark$$

15.17

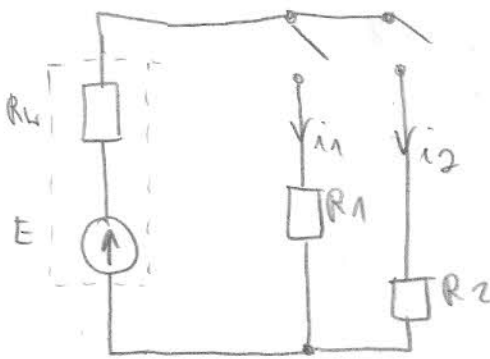

Dane:

$$i_1 = 0,6 \text{ A} \quad R_1 = 2 \Omega$$

$$i_2 = 0,1 \text{ A} \quad R_2 = 14,5 \Omega$$

$$i_1 = \frac{E}{R_W + R_1}$$

$$i_2 = \frac{E}{R_W + R_2}$$

$$U = E - i_1 \cdot R_W$$

$$U = E - i_2 \cdot R_W$$

$$E = i_1 \cdot R_1 + i_1 \cdot R_W$$

$$E = i_2 \cdot R_2 + i_2 \cdot R_W$$

$$E = i_1 \cdot R_1 + i_1 \cdot R_W = i_2 \cdot R_2 + i_2 \cdot R_W$$

$$E = i_1 \cdot R_W - i_2 \cdot R_W = i_2 \cdot R_2 - i_1 \cdot R_1$$

$$R_W (i_1 - i_2) = i_2 \cdot R_2 - i_1 \cdot R_1$$

$$R_W = \frac{i_2 \cdot R_2 - i_1 \cdot R_1}{i_1 - i_2}$$

$$R_W = \frac{1 \cdot 14,5 - 1,2}{0,6 - 0,1} = \frac{0,25}{0,5} = \frac{1}{4} \cdot \frac{2}{1} = \frac{1}{2}$$

$$R_W = 0,5 \Omega \quad \checkmark$$

$$E = i_1 \cdot R_1 + i_1 \cdot R_W$$

$$E = 1,2 + 0,6 \cdot 0,5$$

$$E = 1,2 + 0,3$$

$$E = 1,5 \text{ V} \quad \checkmark$$